

NYCU-EE VLSI 2025

Final Project

6-bit ALU Layout

Data Preparation

1. Extract test data from TA's directory:

```
% tar xvf ~ea25vlsiintroTA01/2025_UMC018_FP.tar
```

2. The extracted LAB directory contains:

2025_UMC018

- ...
- HSPICE/Final_Project/PRE
 - ALU6.sp
- Calibre
 - DRC/BASE/G-DF-Mixed_Mode_RFCMOS18-1.8v_3.3v-1P6M-MMC-Calibre-DRC-2.16_P1.drc
 - LVS/G-DF-MIXED_MODE_RFCMOS18-1.8V_3.3V-1P6M-MMC_CALIBRE-LVS-2.1-P8.txt b.
 - XRC/G-DF-MIXED_MODE_RFCMOS18-1.8V_3.3V-1P6M-MMC_CALIBRE-LVS-2.1-P8.txt
- 09_SUBMIT
 - ALU6_period.txt
 - ./00_tar
 - ./01_submit 1st_demo/2nd_demo
 - ./02_check 1st_demo/2nd_demo

Design Description

Your tasks for this project are:

(1) Implement the 6-bit ALU in HSPICE and perform the pre-simulation


(2) Complete the layout and run the post-simulation.

◆ 6-bit ALU

The ALU takes two 6-bit operands, A[5:0] and B[5:0], along with a 3-bit function select signal, SEL[2:0], which specifies the operation to be performed. The result of the selected operation is provided on the 7-bit output signal, OUT[6:0].

Input signals: A[5:0], B[5:0] and SEL[2:0]

Output signal: OUT[6:0]

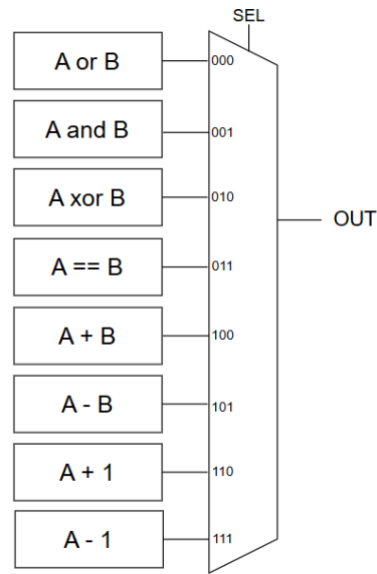

1. Function Description:

1. **A OR B (SEL = 000₍₂₎)**
Performs bitwise OR. OUT[6] is padded with zero.
2. **A AND B (SEL = 001₍₂₎)**
Performs bitwise AND. OUT[6] is padded with zero.
3. **A XOR B (SEL = 010₍₂₎)**
Performs bitwise XOR. OUT[6] is padded with zero.
4. **A == B (SEL = 011₍₂₎)**
Perform the equality operator: if A == B, OUT=0000001₍₂₎; otherwise, OUT=0000000₍₂₎.
5. **A + B (SEL = 100₍₂₎)**
Performs **unsigned** addition of operands A and B. OUT[6] is the carry-out bit.
6. **A - B (SEL = 101₍₂₎)**
Performs **unsigned** subtraction of operands A and B.
OUT[6:0] should be represented as 2's complement.
Ex. A=100011₍₂₎ (35₍₁₀₎), B=110010₍₂₎ (50₍₁₀₎)
=> OUT=1110001₍₂₎ (-15₍₁₀₎)
7. **A + 1 (SEL = 110₍₂₎)**
Performs A + 000001₍₂₎. OUT[6] is the carry-out bit. Operand B is treated as don't care.
8. **A - 1 (SEL = 111₍₂₎)**
Performs A - 000001₍₂₎. OUT[6] is the carry-out bit. Operand B is treated as don't care.

Grading Policy

A. HSPICE and pre-simulation

1. Functional validity of pre-simulation (20%)

All test cases must pass, and the period must be ≤ 4 ns. Otherwise, you will not receive the points for A and B.

B. Layout and post-simulation

1. DRC/LVS (30%)

You must pass **both DRC and LVS**.

2. Performance (30%)

$$\text{Perf} = \frac{1}{\text{Period} \times \text{Area}}$$

◆ *Performance points will only be awarded if DRC/LVS and all test cases pass, and will be ranked from smallest to highest.*

◆ *Eg. Largest perf get 30 %, Second smallest get $\frac{30\%}{\text{\# of passed person}}$.*

C. Poster (20%)

1. Describe the architecture of your ALU design and explain how you optimized your circuit.
2. At least one person in your team need to present the poster fair and explain your structure.
3. The date, location and more information will be announced on E3 soon.

Note

1. Do not modify your ALU6.sp before line 60. Otherwise, your design may fail during demo.


```
1 *****Don't touch settings below*****
2 *****
3 *****
4 ***.....***
5 *** input vector ***
6 ***.....***
7 .VEC 'input.vec'
8 ***.....***
9 *** setting ***
10 ***.....***
11 .lib "uc018.1" LIB/18V.IT
12 .TEMP 25
13 .op
14 .options post
15 *****
16 *** power/input ***
17 ***.....***
18 global VDD GND
19 .param supply=1.8
20 .param load=10f
21
22
23 VDD GND 0 0
24 VDD VDD GND supply
25 *****
26 *** simulation ***
27 *****
28 .tran 0.005n 'period*100'
29 *****
30 *** simulation ***
31 *****
32 .meas tran avg I(VDD) from=0 to='period*100'
33 .meas Pavg param=abs(Iavg)*supply
34 *****
35 *** loading ***
36 ***.....***
37 C0 OUT0 GND load
38 C1 OUT1 GND load
39 C2 OUT2 GND load
40 C3 OUT3 GND load
41 C4 OUT4 GND load
42 C5 OUT5 GND load
43 C6 OUT6 GND load
44 *****
45 *****Don't touch settings above*****
46 *****
47 *****
```

2. Definition of period:

Represents the fixed time interval between two consecutive input vectors.

However, **the output is checked at $0.5 * \text{period}$.**

 For example, with a period of **4 ns**, an input test vector is provided every **4 ns**, and TA will check whether your output is correct every **2 ns** after each input is applied. In other words, the delay of the critical path of the circuit should be less than $0.5 * \text{period}$, that is 2ns in the example.



You can modify the period value in the ALU6.sp and input.vec.

```
**** you can modify period here, remember this period need to match the period in the input.vec ****
**** OUT0~OUT6 should be correct before  $0.5 * \text{period}$  ****
.param period = 1.8n
```

in ALU6.sp

```
;you can modify period and odelay( $0.5 * \text{period}$ ) here, remember this period need to match the period in the ALU6.sp
;OUT0~OUT6 should be correct before  $0.5 * \text{period}$ 
period 1.8
odelay 0.9
```

in input.vec

You must modify the period value in both files, and set $\text{odelay} = 0.5 * \text{period}$.

The minimum precision for the period is 0.01 ns (0.005ns for odelay).

3. You can verify your answer is correct inside the ALU6.err0/ ALU6_post.err0 file.

If it is correct, the ALU6/ALU6_post.err0 file should be empty. **If there is error information in the ALU6/ALU6_post.err0 file, you will fail this project.**

```
1
2 ***** temperature = 25.000000 *****
3 Time      Signal      Simulated  Expected
4 =====
5
```


```
1
2 ***** temperature = 25.000000 *****
3 Time      Signal      Simulated  Expected
4 =====
5 6.300000e-09 OUT2      1          0
6 7.700000e-09 OUT6      0          1
7 7.700000e-09 OUT5      0          1
8 7.700000e-09 OUT2      0          1
9 1.750000e-08 OUT2      1          0
10 1.890000e-08 OUT6      1          0
11 1.890000e-08 OUT2      0          1
12 2.870000e-08 OUT6      1          0
13 2.870000e-08 OUT2      1          0
14 3.010000e-08 OUT2      0          1
15 3.990000e-08 OUT5      0          1
16 3.990000e-08 OUT4      0          1
17 3.990000e-08 OUT2      1          0
18 4.130000e-08 OUT2      0          1
19 5.110000e-08 OUT6      0          1
20 5.110000e-08 OUT5      1          0
21 5.110000e-08 OUT2      1          0
22 5.250000e-08 OUT2      0          1
23 6.230000e-08 OUT2      1          0
24 6.370000e-08 OUT2      0          1
```

Pass

Fail

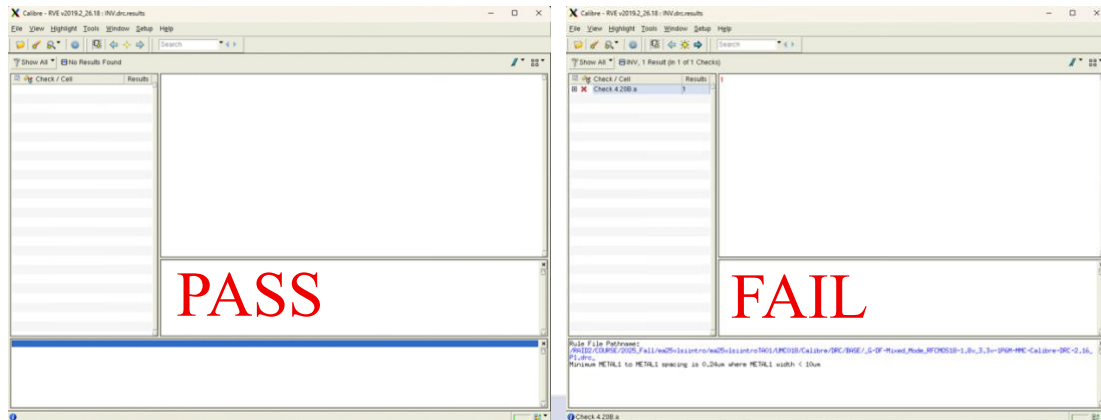
4. DRC rule file: 2025_UMC018/Calibre/DRC/BASE/G-DF-Mixed_Mode_RFCMOS18-1.8v_3.3v-1P6M-MMC-Calibre-DRC-2.16_P1.drc

If there is any drc violation, you will fail this project. e.g.



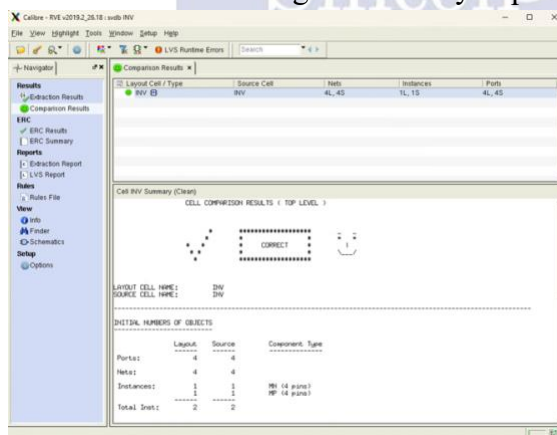
5. LVS rule file: 2025_UMC018/Calibre/LVS/G-DF-MIXED_MODE_RFCMOS18-1.8V_3.3V-1P6M-MMC_CALIBRE-LVS-2.1-P8.txt

You should see smiling face when you pass LVS. e.g.




6. PEX rule file: 2025_UMC018/Calibre/XRC/G-DF-MIXED_MODE_RFCMOS18-1.8V_3.3V-1P6M-MMC_CALIBRE-LVS-2.1-P8.txt


xRC Error should equal 0

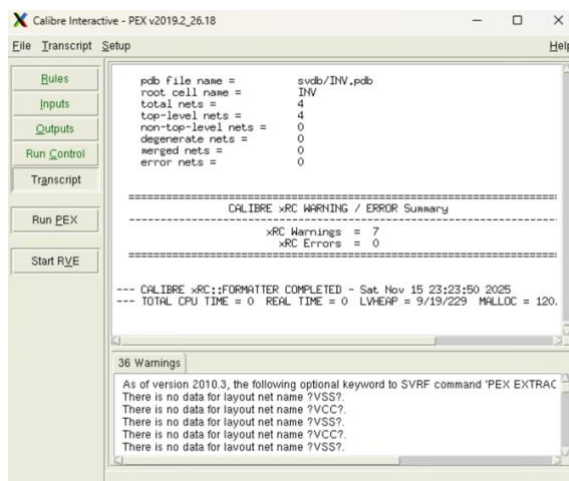

 7. You should paste the pin declaration from .pex.netlist file.
8. The name of the top-module of the submitted GDS should be ALU6
(We strongly recommend you to use the ALU6 cellview which we have already created inside library VLSI)
9. To stream out the GDS file please follow the following steps.
 - a. Go to virtuoso log GUI. Select File-> Export -> Stream



- b. Enter the following information

 

Stream File: 2025_UMC018/ALU6.gds

Library: The library that contains your ALU6 layout


Top cell(s): ALU6


View(s): layout

Technology Library: UMC_18_CMOS

Layer Map: 2025_UMC018/ UMC_18_CMOS/ UMC_18_CMOS.layermap

- c. Confirm that there isn't any error

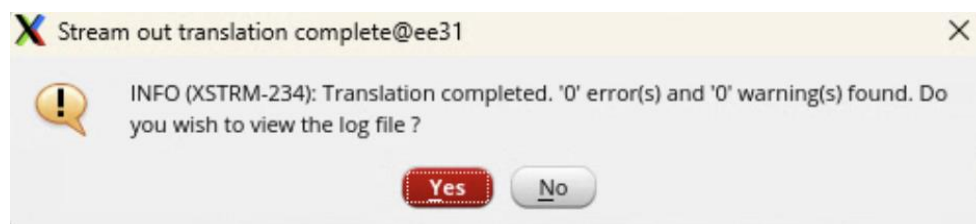


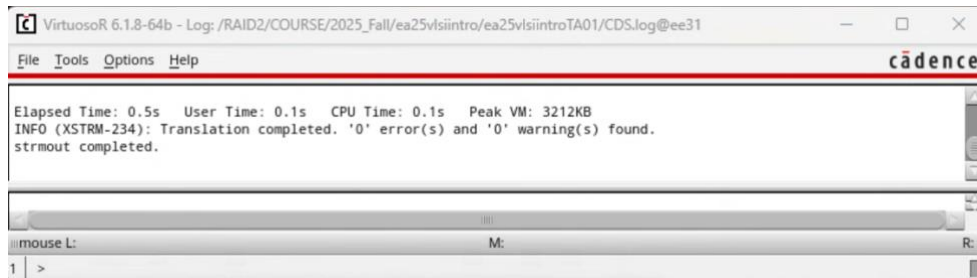


d. Stream in the GDS file back into Virtuoso and make sure it is the same as what you submit.

10. To stream in the GDS file into Virtuoso

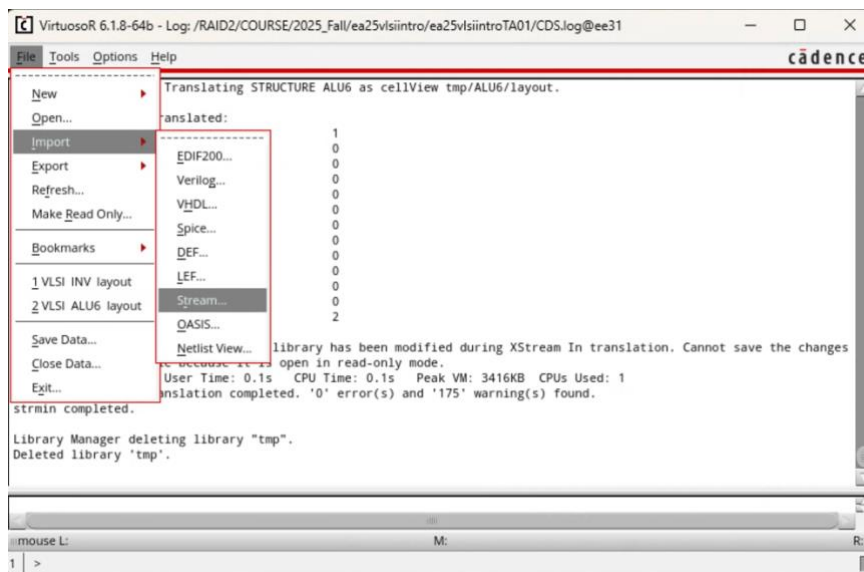a. Go to virtuoso log GUI. Select File-> Import -> Stream



b. Type in the following information

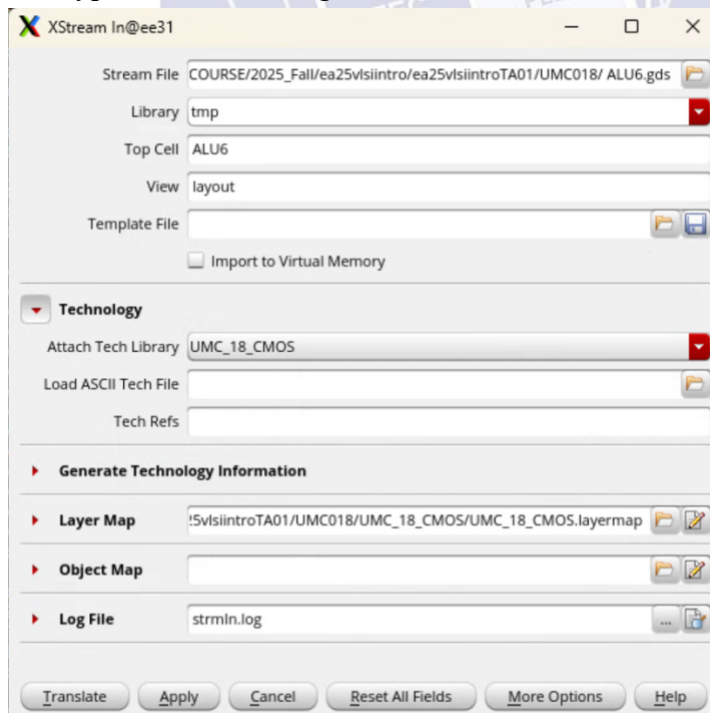

Stream File: Path of your GDS file

Library: A **NEW** library that you want to store your ALU6 layout


Top cell(s): ALU6

View(s): layout


Technology Library: UMC_18_CMOS

Layer Map: 2025_UMC018/ UMC_18_CMOS/ UMC_18_CMOS.layermap


c. Confirm that there isn't any error

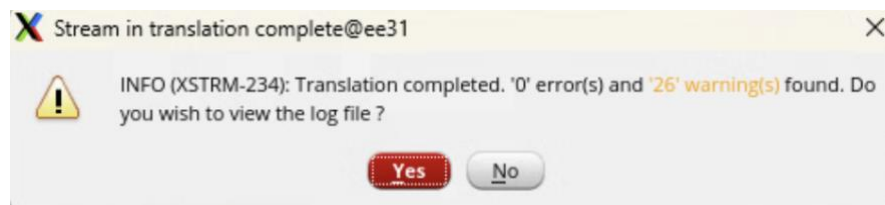

 11. Make sure labels inside your layout don't exceed your layout boundary.



Demo area will cover label box

-> Larger area than expect 

Good 

Submission Rules

1. **Only Member1** on the team list need to submit the file.
2. Please submit your files under 09_SUBMIT before 12:00 at noon:
Due Day: **1st Demo: 12/29 12:00** **2nd Demo: 12/31 12:00 (30% off)**
If uploaded files **violate the naming rule**, you will get **5 deduct points**

- In this project, you can adjust your period time in “09_submit/ALU6_period.txt”. It means that the TA will demo your design under this period:
Ex. “Pre-sim period:2.48” No space or any other character is allowed in the txt file.

```
Pre-sim period:
Post-sim period:
```

- Before executing ./00_tar inside 09_submit folder, you should make sure the following files are in the following folder
 - **Pre-sim Hspice:** 2025_UMC018/HSPICE/Final_Project/PRE/ALU6.sp
 - **GDS:** 2025_UMC018/ALU6.gds
 - **Period txt:** 2025_UMC018/09_submit/ALU6_period.txt
- After executing ./00_tar and ./01_submit, make sure to use 02_check command like the figure below and untar the file to check if all the files are uploaded or not.

```
[Exercise/09_SUBMIT]% ./02_check 1st_demo
```

Example:

The downloaded tar file should contain **ALU6_ea25vlsiintro999.sp, ea25vlsiintro999_period.txt, and ALU6_ea25vlsiintro999.gds**

If the uploaded files violating the naming rule, you will get **5 deduct points**.

If you omit any file, you will fail demo.

3. Template folders and reference commands:

2025_UMC018

ALU6.gds

HSPICE/Final_Project/PRE/

ALU6.sp

09_SUBMIT/ (submit your files):

ALU6_period.txt

./00_tar

./01_submit 1st_demo/2nd_demo

./02_check 1st_demo/2nd_demo